

Verilog Synthesis

Recall: only subset of Verilog is synthesizable.

Blocking Versus Non-Blocking assignments in synchronous blocks

The choice affects both simulation and hardware synthesis.

blocking: evaluated one after another


non-blocking: evaluated simultaneously

<pre>always @ (posedge clk) begin c = a; b = c; end</pre>		NOK	// at posedge, always non-blocking
<pre>always @ (posedge clk) begin e <= d; f <= e; end</pre>		OK	always @(posedge clk) begin c <= a; b <= a; end
<pre>always @ (posedge clk) begin a <= 1'b0; if (en == 1'b1) a <= b; end</pre>		OK, but should be avoided	
<pre>always @ (posedge clk) begin if (en == 1'b1) a <= b; else a <= 1'b0; end</pre>		OK	"<=" is the main difference between SW and HW design

2

D-flop w/ Synchronous Reset

 
- assume that reset is active low. res_n another common name



```
always @(posedge clk) begin
  if (!res_n)
    q <= 0;
  else
    q <= data;
end
```

D-flop w/ Asynchronous Reset

 - assume that reset is active low. res_n another common name
- most basic FPGA libraries provide asynchronous FFs which have additional reset signals. they are preferable



```
always @(posedge clk or negedge res_n) begin
  if (!res_n)
    q <= 0;
  else
    q <= data;
end
```

If/else in Verilog

- must have a begin/end keyword set if it surrounds multiple lines
- must be in an always or initial block

[If/else example: Flip-Flop, reset used as asynchronous signal]

```
always @(posedge clk or negedge res_n) begin
    if (!res_n)
        begin
            q1 <= 0;
            q2 <= 0;
        end
    else
        begin
            q1 <= data1;
            q2 <= data1;
        end
end
```

Multiplexer: Implemented with if/else

- multiplexors are a combinatorial logic unit, so they are not driven by a clock
- multiplexors are synthesized into custom FPGA/ASIC hardware
- multiplexors use blocking assignments because their output is continuously updated
- most efficiently implemented with transmission gates

```
always @(*) begin
    if (sel)
        z = in1;
    else
        z = in0;
end
```

Larger Multiplexers

- larger multiplexors are used to “decode” select signals in the if statement
- sometimes hierarchies of multiplexers are used b/c there is hardware for 2-1, 4-1, 8-1
 - synthesis tools will come up with the minimal logic to implement large if/else statements as a mux

[Example: if/else synthesized into a 4-1 mux]

```
always @(*) begin
    if (sel==2'b00)
        z = in0;
    else if (sel==2'b01)
        z = in1;
    else if (sel==2'b10)
        z = in2;
    else
        z = in3;
end
```

[Example: if/else synthesized into ?]

- may synthesize into not a mux.

```
always @(*) begin
  if (sel==2'b00)
    z = in0;
  else if (sel==2'b01)
    z = in1;
  else
    z = in2;
end
```

For larger muxes, a case statement looks better!

Multiplexer: implemented with Case

- often synthesized into hardware just like the if/else
- default case is a useful way to handle unknown cases

[Example: equivalent Case and If/Else statements]

the default case body cannot be synthesized, so it would be ignored in hardware implementation

```
wire [15:0] in0, in1, in2, in3;
wire [1:0] sel;
always @(*) begin
  case ( sel )
    2'b00: Y = in0;
    2'b01: Y = in1;
    2'b10: Y = in2;
    2'b11: Y = in3;
    default: Y = 16'hxxxx;
  endcase
end
```

```
always @(*) begin
  if (sel==2'b00)
    z = in0;
  else if (sel==2'b01)
    z = in1;
  else if (sel==2'b10)
    z = in2;
  else if (sel==2'b11)
    z = in3;
  else
    z = 1'bx;
end
```

Design pattern:
Always have a else/default
case to catch bugs. Assign
x'es

Casex in Verilog

- casex statements use the equivalent of === to do comparisons (z and x are well-defined inputs)
 - casex treats x, z, or ? as don't cares
 - casez treats z or ? as don't cares

[Example]

default case would have been sufficient for the last case listed.

```
always @ (*)
casex (sel)
  0 : y = a;
  1 : y = b;
  2 : y = c;
  3 : y = d;
  2'bx, 2'bx0, 2'bx1, 2'b0x, 2'b1x,
  2'bzz, 2'bz0, 2'bz1, 2'b0z, 2'b1z : $display("Error in SEL");
endcase
```

For Loop in Verilog: not what it seems

In software, for loops are used as a dynamic construct to perform an action multiple times. In hardware design, for loops generate multiple components that are defined within the body.

- dynamic enabling/disabling of hardware is not possible
- wires can be used to interconnect the repeated hardware
- to synthesize, the loop boundary must be a compile time constant

[Example: For Loop]

- generates 4 multiplexers with an XOR going into each, 1 for each bit of b and c

```
integer i;
for(i=0 ; i <4 ; i++ ) begin
    if(d[i])
        a[i] = b[i] ^ c[i];
    else
        a[i] = 0;
end
```

is this synthesizable?

Local Parameters in Verilog

- local parameters are something from the old Verilog-95 style
- used for inputs
- increase flexibility of modules

[Example: local parameters]

- A_size can be changed during instantiation, but B_size cannot

```
module first_module
#(parameter A_size = 4)(A, B);
    localparam B_size = 1<<A_size;
    input [A_size-1:0]A;
    input [B_size-1:0]B;
    output C;
    ...
endmodule
```

Compiler Directives

- used to let the compiler know what to do

```
`include "file_name" // defines, paremeters definitions

`ifdef macro_name
    // verilog_source_code
`else
    /* verilog_source_code */
`endif

`define VAL 1'b1
`define NAND(dval) nand #(dval)

`NAND(3) i1 (y,a,`VAL);
`NAND(5) i2 (o,c,d);
```

Interfaces vs. Protocols

- Verilog modules define interface but not protocol on how to use them ☹️
 - this is a weakness of Verilog!
- C/C++ has similar issues (lack of protocol) but protocol is more critical in HDLs
- Challenge: how should we use the interface?
 - Solution: Module interface + written specification + timing diagram

[Example: DRAM]

Written Specification for the Module:

- each access starts with a RAS
 - wait for ras2cas
 - assert CAS
- the only thing to clearly describe how the module works is to see the timing diagram.
 - protocol missin!



Hardware versus Software Design

- hardware design is always about performance: if you don't need performance, write software. x)
- a significant part of RTL design is about performance tuning

Goal of Hardware Design:

- optimize throughput (operations/second)
- optimize Fmax (clock frequency)

2 options to Optimize Hardware:	
Play with the tools (synthesis constraints, place and route P&R)	Modify hardware design (more powerful technique)
<ul style="list-style-type: none"> constrain the design to a target frequency synthesis will try to meet timing synthesis will also optimize for area/power constrain tighter to push timing.	pipelining: split combinatorial logic blocks and insert FFs in between them so that the design can be clocked higher <ul style="list-style-type: none"> 2 cycles but 2x max frequency means double throughput

Many hardware designs have 100s-1,000s of pipeline stages.

Quick Frequency Clock

- if design does not meet your targets, you need to redesigns

Chicken-egg problem: no design, no timing. No timing, no design

Solution: design/implement the pipeline stage that seems the most frequency constrained, or or the pipeline stage that “if changed” would significantly modify other sections designs.

→ get a sense of what hardware can go into an x ns propagation delay.
get a feeling for computational complexity of particular operators.

Synthesis

Synthesis can take a loooong time for larger designs.

Problem:

You do not know the frequency you can clock at until you synthesize.

Solution:

synthesize frequently. Learn to love the warnings that tools give – it will simplify your testing!
You should have 0 warnings, or understand the reason for a warning.

Clock Signal (P&R)

Recall there are 3 types of signals in hardware design:

1. data
2. clock
3. reset

clock and reset are driven across the whole chip to drive each and every flip flop.

when doing FPGAs

- specify the specialty of clk and reset
- drive clock signal from a BUFG (buff global clock)
- any synchronous block must be driven by clock buffer BUFG

Driving the clock signal from a BUFG is needed to minimize skew

- clock signal is fanned out and distributed, leading to clock skew
- low skew is desirable because of setup/hold time of FFs.
 - design has to be clocked at rate that accommodates clock skew and logic latency
 - positive and negative skew possible
 - low skew helps phase match off-chip synchronous signals.
 - some signals from previous FFs might clock inappropriately
 - high skew means clock period must be increased

Generating a Clock for Test Benches

Clock signals can be generated in an initial block in testbenches. not synthesizable. Below are some examples of how to do for a clock period of 10 time units.

```
reg clk;
```

```
// method 1
initial begin
  clk = 0;
end
always
  #5 clk <= ~clk;
```

```
// method 2
always
  begin
    #5 clk = 0;
    #5 clk = 1;
  end
```

```
// method 3
initial begin
  clk = 0;
  forever begin
    #5 clk = ~clk;
  end
end
```

Reading Timing Reports

Timing Report: Synopsys

Pictured below is a timing report from Synopsys, a big company that built tools people use. Synthesis tools will make multiple designs and list the following for each:

- area
- worst negative slack
- total negative slack
- design rule cost

ELAPSED TIME	AREA	WORST NEG SLACK	TOTAL NEG SLACK	DESIGN RULE COST	ENDPOINT
0:00:37	407904.9	0.00	0.0	137.5	
0:00:45	263602.4	1.70	708.8	148.5	
0:00:49	264357.0	0.55	152.1	140.1	
0:00:52	264336.9	0.38	41.0	139.1	
0:00:56	265694.2	0.04	0.8	139.1	
0:01:01	266379.2	0.00	0.0	27.4	

Point	Incr	Path
clock clk (rise edge)	0.00	0.00
clock network delay (ideal)	0.17	0.17
mdu/rsrv_mdu/vj_dff/q_reg[3]/CLK (fdf1c3)	0.00 #	0.17 r
data arrival time		3.36
clock clk (rise edge)	3.33	3.33
clock network delay (ideal)	0.17	3.50
fpalul_rsrv/rsrv_fsm/curr_state_reg[0]/CLK (fdef2c6)	0.00	3.50 r
library setup time	-0.14	3.36
data required time		3.36
data required time		3.36
data arrival time		-3.36
slack (MET)		0.00

How can you trade-off
Area vs. slack again?

slack

- slack == clock period – propagation delay
- 0 slack is good. worst negative slack is positive and means design could be clocked faster.

How can you trade-off area and slack?

Timing Report: Xilinx

Xilinx is another company that has synthesis tools that will have a report. Reports most critical paths in design, source, clock, etc.

```
Timing Detail:
-----
All values displayed in nanoseconds (ns)

-----
Timing constraint: Default period analysis for Clock 'clk'
Delay:            8.082ns (Levels of Logic = 2)
Source:           sixty_lsbcount_qoutsig_0
Destination:      sixty_msbcount_qoutsig_2
Source Clock:     clk rising
Destination Clock: clk rising

Data Path: sixty_lsbcount_qoutsig_0 to sixty_msbcount_qoutsig_2

Cell:in->out      fanout    Gate    Net
                  Delay      Delay    Logical Name (Net Name)
-----
FDCPE:c->q        9         1.085   1.908   sixty_lsbcount_qoutsig_0
(sixty_lsbcount_qoutsig_0)
LUT4:i0->o        6         0.549   1.665   sixty_lsbcount__n00011
(sixty_lsbcount__n0001)
LUT3:i2->o        4         0.549   1.440   sixty_msbcel (sixty_msbce)
FDCPE:ce          0.886     sixty_msbcount_qoutsig_2
-----
Total              8.082ns(3.069ns logic,5.013ns route)
                  (38.0% logic, 62.0% route)
```

Resource Report: Synopsys

```
...
Number of ports:      387
Number of nets:       1515
Number of cells:      153
Number of references: 29

Combinational area:   104070.601562
Noncombinational area: 157332.781250
Net Interconnect area: undefined (Wire load has zero net area)

Total cell area:      261400.375000
Total area:           undefined
...
```

Other Statistics: Synopsys

```
...
Current design is 'dynamic_schd'.
Design      : _sel21
Ports       : 387 (in:178 out:209 inout:0)
Cells       : 14915
Hierarchical : 178
Leaf        : 14737
Sequential  : 3188 (latch:128 ff:3060 ms:0)
Combinational : 11549
...
```

class projects should not have latches

Why?

Latches probably mean you forgot to flop a signal
E.g. Include all the branches of an if or case statement.

Resource Report: Xilinx

```
Design Statistics
# IOS                      : 27

Macro Statistics :
# ROMs                : 3
#   16x10-bit ROM     : 1
#   16x7-bit ROM      : 2
# Counters            : 2
#   4-bit up counter  : 2

Cell Usage :
# BELS                : 59
#   GND                : 1
#   LUT2               : 2
#   LUT3               : 9
#   LUT4               : 30
#   MUXCY              : 8
#   VCC                : 1
#   XORCY              : 8
# FlipFlops/Latches   : 14
#   FDC                : 5
#   FDCPE              : 8
#   FDP                : 1
# Clock Buffers        : 1
#   BUFGP              : 1

# IO Buffers          : 26
#   IBUF               : 2
#   OBUF               : 24
# Others               : 1
#   tenths             : 1
=====

Device utilization summary:
-----

Selected Device : 2s15cs144-6

Number of Slices:                25 out of 192    13%
Number of Slice Flip Flops:      14 out of 384    3%
Number of 4 input LUTs:          41 out of 384   10%
Number of IOBs:                  26 out of 96    27%
Number of TBUFs:                  0 out of 192    0%
Number of BRAMs:                  0 out of 4      0%
Number of MULT18X18s:             0 out of 4      0%
Number of GCLKs:                   1 out of 4     25%
```