 


## Linear Feedback Shift Registers

LFSRs (Linear Feedback Shift Registers) are frequently used to produce pseudo-random sequences of bits using XOR gates and Flip Flops. LFSRs have low overhead in hardware because they only use XOR gates to generate new bits. Two implementations of an 8-bit LFSR can be found in this folder: one implemented with **structural Verilog** and one implemented with **behavioral Verilog**. Figure 1 depicts the design of the LFSR.



Timing and Resource Analysis: lfsr_8b_behav & lfsr_8b_struc	
Specified clock period	400ns
Worst Negative Slack <b>WNS</b>	398.861ns
Minimum clock period <b>Tmin</b>	1.139ns
Maximum clock frequency <b>Fmax</b>	0.87796 GHz
# look up tables <b>LUT</b>	5
# of registers	8

The timing and resource reports for both implementations yielded the same results.